

# RL AC Circuit: Frequency

